

# ECE 4750 Computer Architecture, Fall 2021

## Lab 3: Blocking Cache

School of Electrical and Computer Engineering  
Cornell University

revision: 2021-10-21-19-33

In this lab, you will design **two finite-state-machine (FSM) cache microarchitectures**, which we will eventually compose with the processor designs you developed in the previous lab. **The baseline design is a direct-mapped, write-back, write-allocate cache**, and **the alternative design is a two-way set associative cache that should reduce the miss rate by avoiding conflict misses**. You are required to implement the baseline and alternative designs, verify the designs using an effective testing strategy, and perform an evaluation comparing the two implementations. **As with all lab assignments, the majority of your grade will be determined by the lab report. You should consult the course lab assignment assessment rubric for more information about the expectations for all lab assignments and how they will be assessed.**

This lab is designed to give you experience with:

- basic memory system design;
- complex finite-state-machine cache controllers;
- microarchitectural techniques for implementing cache associativity;
- abstraction levels including functional- and register-transfer-level modeling;
- design principles including modularity, hierarchy, and encapsulation;
- **design patterns** including message interfaces, control/datapath split, and FSM control;
- agile design methodologies including incremental development and test-driven development.

This handout assumes that you have read and understand the course tutorials and the lab assessment rubric. To get started, you should access the ECE computing resources and you should have used the `ece4750-lab-admin` script to create or join a GitHub group. If you have not do so already, source the setup script and clone your lab group's remote repository from GitHub:

```
% source setup-ece4750.sh
% mkdir -p ${HOME}/ece4750
% cd ${HOME}/ece4750
% git clone git@github.com:cornell-ece4750/lab-groupXX
```

where XX is your group number. **You should never fork your lab group's remote repository! If you need to work in isolation then use a branch within your lab group's remote repository.** If you have already cloned your lab group's remote repository, then use `git pull` to ensure you have any recent updates before running all of the tests. You can run all of the tests in the lab like this:

```
% cd ${HOME}/ece4750/lab-groupXX
% git pull --rebase
% mkdir -p sim/build
% cd sim/build
% py.test ../lab3_mem
```


All of the tests for the provided functional-level model should pass, while the tests for the baseline and alternative cache designs should fail. For this lab, you will be working in the `lab3_mem` subproject which includes the following files:

- `BlockingCacheFL.py` – FL cache
- `BlockingCacheBaseDpathVRTL.v` – Verilog blocking direct-mapped cache's datapath
- `BlockingCacheBaseCtrlVRTL.v` – Verilog blocking direct-mapped cache's control unit
- `BlockingCacheBaseVRTL.v` – Verilog blocking direct-mapped cache
- `BlockingCacheBaseRTL.py` – Wrapper to choose which RTL language
- `BlockingCacheAltDpathVRTL.v` – Verilog blocking set-associative cache's datapath
- `BlockingCacheAltCtrlVRTL.v` – Verilog blocking set-associative cache's control unit
- `BlockingCacheAltVRTL.v` – Verilog blocking set-associative cache
- `BlockingCacheAltRTL.py` – Wrapper to choose which RTL language
- `mem-sim` – Cache simulator for evaluation
- `mem_sim_eval.py` – Script to run all patterns on each design
- `__init__.py` – Package setup
- `test/BlockingCacheFL_test.py` – FL cache unit tests
- `test/BlockingCacheBaseRTL_test.py` – Direct-mapped cache unit tests
- `test/BlockingCacheAltRTL_test.py` – Set-associative cache unit tests
- `test/TestCacheSink.py` – Custom test sink for cache
- `test/__init__.py` – Package setup


## 1. Introduction

Accessing main memory can require hundreds of cycles, but cache memories can significantly reduce the average memory access latency for well-structured address patterns. Caches are faster than main memory because they are smaller and are located close to the processor; but because a cache can only hold a subset of all memory locations at any one time, we must carefully manage what data we keep in the cache. A cache hit occurs when the data we are requesting is already in the cache, while a cache miss occurs when the data we are requesting is not in the cache and thus requires accessing main memory. Caches exploit spatial and temporal locality to increase the number of cache hits. In an address pattern with significant spatial locality, if we access a given address then in the near future, we are likely to access an address close to the first address. In an address pattern with significant temporal locality, if we access a given address then in the near future, we are likely to access that same address again. In this lab, you will implement and evaluate two cache microarchitectures that organize cache lines in two different ways: (1) direct-mapped where every cache line can only be placed in a single location in the cache, and (2) **two-way set-associative** where every cache line can be placed in one of two locations in the cache. Both caches will use **a write-back, write-allocate policy** for handling write misses. Additionally, both caches will have the ability to act as a bank in a larger multi-bank cache organization.

We have provided you with a functional-level model of a cache, which essentially just passes all cache requests through to the memory interface, and passes all memory responses through to the cache response interface. **While this might not seem useful, the functional-level model will enable us to develop many of our test cases with the test memory before attempting to use these tests with the baseline and alternative designs.**

 


**Figure 1:** Memory System - The cache is integrated with a test source, test sink, and test memory for testing and evaluation.

 

**Figure 2: Cache and Memory Request/Response Message Formats** – Cache request/response messages are sent between the processor and cache and contain four bytes of data (i.e., one word), while memory request/response messages are sent between the cache and the test memory and contain 16 bytes of data (i.e., one cache line).

Figure 1 shows a block-level diagram illustrating how the functional-level, baseline, and alternative designs are integrated with a test source, test sink, and test memory for testing and evaluation. We will load data into the test memory before resetting the cache. Once we start the execution, the test source will send memory requests into the cache, and eventually the cache will send memory responses to the test sink. If the cache needs to access main memory, then the cache will send memory requests to the test memory, and eventually the test memory will send memory responses back to the cache. We make extensive use of the latency insensitive val/rdy **micro-protocol** in the cache interface. There are four different val/rdy channels.

- **cachereq** : from test source (processor) to cache
- **cachresp** : from cache to test sink (processor)
- **memreq** : from cache to test memory
- **memresp** : from test memory to cache

 

**Figure 3:** Banked Cache Organization - Four-bank cache organization. Highlighted path is for a memory request that hits in bank 0.

Address With No Banking

31	8	7	4	3	0
tag				index	offset

Address With Four Banks

31	10	9	6	5	4	3	0
tag			index	bank	offset		

**Figure 4:** Memory Address Formats With and Without Banking - When using the baseline or alternative design as a bank in a larger cache, we need to exclude the bank bits when indexing in the cache since the request network will take care of routing messages to the correct bank.

The message formats for memory requests and responses are shown in Figure 2. Corresponding PyMTL BitStructs are defined in pclib here:

- <https://github.com/cornell-brg/pymtl/blob/ece4750/pclib/ifcs/MemMsg.py>

Similar Verilog structs are defined in `vc/mem-msgs.v` included within the lab release. Memory requests use fields to encode the type (e.g., read, write, init), the address, the length of data in bytes, and the data. Memory responses use fields to encode the type (e.g., read, write), the length of data in bytes, and the data. The opaque field can be used for implementation defined behavior. **You should always ensure the opaque field is correctly preserved in the response.** Note that the memory messages used for the `cachereq` and `cacheresp` interfaces are for a single word (i.e., 32-bit data field and 2-bit length field), while the memory messages used for the `memreq` and `memresp` interfaces are for an entire cache line (i.e., 128-bit data field and 4-bit length field). If the length field is one then only the least significant byte of the data field (i.e., bits 7-0) is valid. If the length field is two then only the least significant two bytes of the data field (i.e., bits 15-0) are valid. If the length field is zero then all bytes are valid. Note that while the memory message format is quite flexible, our cache designs will only support 4-byte cache requests and 16-byte memory requests. The data field can contain an arbitrary value in a write memory request, however *the data field must contain all zeros in a write memory response*. This simplifies creating reference responses when testing. We add a two-bit test field to each `cacheresp` and `memresp` message. **We use the test field in `cacheresp` for testing. If a `cachereq` ends up with a cache miss, we should set the corresponding `cacheresp` message's test field to be `2'b0`. If a `cachereq` turns out to be a cache hit, we should set the corresponding `cacheresp` message's test field to be `2'b1`. By using the test field in the test harness can verify whether a cache transaction is a hit or a miss.**


One way to increase cache bandwidth is to enable a cache to process multiple transactions at the same time. Figure 3 shows an alternative approach based on a *banked cache* organization. In a banked cache, we add a request network which directs a cache request to the appropriate bank based on some bits in the address of this cache request. Cache responses are returned over a different response network. Different cache banks can be potentially execute different transactions at the same time, and this increases the overall throughput of the system. The cache you design in this will be used both on its own (i.e., in a single-bank configuration) as well as in a four-bank configuration. Figure 4 illustrates which bits are used by the request network to direct a given cache request to the appropriate cache bank in a four-bank configuration. For example, if bits 4 and 5 of the cache request address are zero then the cache request is sent to bank zero, and if bits 4 and 5 of the cache request are one then the cache request is sent to bank three. **For a single-bank design to support its use in a banked cache organization, we need to exclude the bank bits when indexing into the cache bank.** In other words, if we consider all four banks holistically as a single “banked cache”, a fourth of the sets of the banked cache are in each bank. Note you cannot completely ignore the bank bits since you will need them when generating a cache line address for refills.

## 2. Baseline Design

The baseline design for this lab is a direct-mapped, write-back, write-allocate cache with a total capacity of 256 bytes, 16 cache lines, and 16 bytes per cache line. As with the earlier labs, we will be decomposing the baseline design into two separate modules: the datapath which has paths for moving data through various arithmetic blocks, muxes, and registers; and the control unit which is in charge of managing the movement of data through the datapath. As in the first lab, the control unit will use an FSM. Because the cache design is significantly more complicated than the first lab, we have decided to place the datapath module, control unit module, and the parent module that connects the datapath and control unit together in three different files.

The datapath for the baseline design is shown in Figure 5. The blue signals represent the control/status signals for communicating between the datapath and the control unit. Your datapath module should probably instantiate a child module for each of the blocks in the datapath diagram; in other words, you should mostly use a structural design style in the datapath. Although you are free to develop your own modules to use in the datapath, you can also use the ones provided for you in the `pclib` and `vclib`. The `repl` block takes a 32b value and simply replicates it four times to create a 128b value. The `mkaddr` block simply concatenates the tag and idx plus some zeros like this: `{tag, 4'b0000 }`. As we become more proficient, we can use our judgement about what needs to be encapsulated in a child module. For example, the `repl` and `mkaddr` blocks can probably be done directly in the datapath without encapsulating them in a module. These operations are just wiring and not really “logic”. **However, we strongly encourage students to use comments and a temporary signal to clearly indicate where in the code you are doing this kind of wiring so that it is still easy to connect your datapath diagram to your code.** Notice that to simplify our design, we are implementing the tag and data arrays using **combinational-read SRAMs**. This means that after setting the read address signals, the read data is available that same cycle. Note that more realistic designs meant for implementation in either an FPGA or ASIC would likely need to synchronous SRAMs.

We provide two kinds of combinational-read SRAMs in both `pclib` and `vclib`: a version that supports partial byte-writes but where each entry must be an even multiple of eight bits (let’s call this `ByteWriteSRAM`) and a version that does not support partial byte-writes but where each entry can be any bitwidth you want (let’s call this `FullWriteSRAM`). We recommend using a `ByteWriteSRAM` for your data array (since you need partial write support, and cache lines are an even multiple of eight bits), and we recommend using a `FullWriteSRAM` for your tag array (since you do not need partial

 

**Figure 5: Baseline Datapath** – Direct-mapped, write-back, write-allocate cache with 16-byte cache lines and a total capacity of 256 bytes. repl = replicate 32b four times to create 128b signal; mkaddr = concatenate { tag, 4'b0000 }. Orange blocks represent extracting or inserting fields into a Verilog struct.

write support, and tags are not necessarily an even multiple of eight bits). Unfortunately, we made this a little more confusing than we had to by using different names for these two different kinds of SRAMs in `pclib` vs. `vcplib`. To make matters worse we also used slightly different interfaces in `pclib` vs. `vcplib`. They have the same functionality though, and remember that all of these SRAMs can only do one read *or* one write per cycle regardless of the interface. So here is the naming:

- ByteWriteSRAM in `pclib` (use for data array)
  - Named: `SRAMBytesComb_rst_1rw`
  - Link: <https://github.com/cornell-brg/pyrtl/blob/master/pclib/rtl/SRAMs.py#L73-L140>
  - addr: address for reads and writes
  - rdata: read data
  - wen: write enable
  - wben: write byte enable
  - wdata: write data

- FullWriteSRAM in pclib (use for tag array)
  - Named: SRAMBitsComb\_rst\_1rw
  - Link: <https://github.com/cornell-brg/pymtl/blob/master/pclib/rtl/SRAMs.py#L9-L71>
  - addr: address for reads and writes
  - rdata: read data
  - wen: write enable
  - wdata: write data
- ByteWriteSRAM in vclib (use for data array)
  - Named: vc\_CombinationalSRAM\_1rw
  - Link: in lab release at vc/srams.v#L88-L176
  - read\_en: read enable
  - read\_addr: read address
  - read\_data: read data
  - write\_en: write enable
  - write\_byte\_en: write byte enable
  - write\_addr: write address
  - write\_data: write data
- FullWriteSRAM in vclib (use for tag array)
  - Named: vc\_CombinationalBitSRAM\_1rw
  - Link: in lab release at vc/srams.v#L8-L86
  - read\_en: read enable
  - read\_addr: read address
  - read\_data: read data
  - write\_en: write enable
  - write\_addr: write address
  - write\_data: write data

The baseline design is direct mapped with 16-byte cache lines and a total capacity of 256 bytes (i.e., 16 cache lines). So we need four bits for the byte offset and four bits for the index leaving 24 bits for the tag. Ideally, this would mean the direct mapped cache can use a FullWriteSRAM with 24 bits. Technically, for a banked-cache organization, we can use even fewer tag bits since the bank bits will always be the same in any given bank. For a four-bank cache organization, we really only need 22 bits for the tag, but we would have to concatenate the bank bits when we do a cache line eviction. Given all of this, in this lab we recommend a simpler approach that wastes a little area in the tag array. Students should always use 28 bits in the tag array (even in the alternative design). This makes the tag array a “tag” array in quotes, since the tag array really stores the tag, the bank bits, and the index. This is fine for our purposes. The datapath diagram in Figure 5 uses the Verilog port names and uses 28 bits in the tag array. If you take this approach, the only change you should need to support banking is to simply choose different bits for the set index based on Figure ??.

 


Figure 6: Baseline FSM Control Unit

The FSM for the baseline design is shown in Figure 6. The control unit should also include additional valid and dirty bits to track the state of each tag entry. You should not use SRAMs for the valid and dirty bits. You should instead use standard register files. We provide register files in `pclib` here:

- <https://github.com/cornell-brg/pymtl/blob/ece4750/pclib/rtl/RegisterFile.py>

The equivalent Verilog register files are defined in `vc/regfiles.v`. The various FSM states are described in more detail below:

- STATE\_IDLE (I) – Receive the incoming cache request and place it in the input registers
- STATE\_TAG\_CHECK (TC) – Check tag, state transition based on hit/miss, valid/dirty
- STATE\_INIT\_DATA\_ACCESS (IN) – Immediately write to appropriate cache line
- STATE\_READ\_DATA\_ACCESS (RD) – Read from appropriate cache line
- STATE\_WRITE\_DATA\_ACCESS (WD) – Write to appropriate cache line
- STATE\_EVICT\_PREPARE (EP) – Read tag and data, and prepare eviction message
- STATE\_EVICT\_REQUEST (ER) – Make a request to memory to write the evicted cache line
- STATE\_EVICT\_WAIT (EW) – Wait for memory response
- STATE\_REFILL\_REQUEST (RR) – Make a request to memory for refill the desired cache line
- STATE\_REFILL\_WAIT (RW) – Wait for memory response
- STATE\_REFILL\_UPDATE (RU) – Write the response to the victim cache line
- STATE\_WAIT (W) – Wait while the sink (processor) is busy

This FSM control unit differs from the basic FSM cache discussed in lecture. This is due to the need to handle the various latency insensitive interfaces, the init transaction, and waiting for eviction



responses. The FSM cache microarchitectures used in this lab will have a hit latency of four cycles (e.g.,  $I \rightarrow TC \rightarrow RD \rightarrow W$ ). In the previous lab, the memory access time was usually a single cycle although you also tested your processor with random delays on the memory interface. Assuming we correctly implement the latency insensitive val/rdy microprotocol in both the processor and cache, then there should be no problem composing these two subsystems. Later optimizations can reduce the cache hit latency without the need to modify the processor.

We strongly encourage you to take an incremental design approach using the following steps:

- Implement the init transaction (I, TC, IN, W)
- Implement the read hit path (I, TC, RD, W)
- Implement the write hit path (I, TC, WD, W)
- Implement the refill path (I, TC, RR, RW, RU, RD/WD, W)
- Implement the evict path (I, TC, EP, ER, EW, RR, RW, RU, RD/WD, W)
- Implement support for banking

The hit path is the simplest place to start, but in order to hit in the cache, we need valid data in the cache. The init transaction (explained further in Section 4) allows you to write data into the cache without doing a refill from main memory. This kind of transaction is an example of *design-for-test* since this transaction is only meant to simplify testing and has no real use once we have a working cache model. We recommend implementing the init transaction first, and then using this transaction to implement and test both hit paths. Once the hit paths are working, then you can move onto the more complicated miss paths.

### 3. Alternative Design

The alternative design for this lab is a two-way set-associative, write-back, write-allocate cache with the same capacity (256 bytes) and cache line size (16 bytes) as the baseline cache. The general FSM for the alternative design will be very similar to that of the baseline design, except that the control signals will likely be different. Note that you will need to split the valid bits into two parts, one for each way and carefully keep track of them. You will need to AND the result of the tag match in each way with the appropriate valid bit to determine if there is a hit or miss. The control unit should use a least-recently-used (LRU) replacement policy to choose between the two ways during eviction. You should track the LRU status with separate bits in the control unit.

### 4. Testing Strategy

**We provide you with a few basic directed tests.** For example, we provide you with a basic test for the read hit path for clean lines. Although you will not need to write as many tests as in the previous lab, the tests for this lab may be more challenging since you will need to carefully craft directed tests that exercise all paths in your datapath and all states and state transitions in your FSM. As with the previous labs, you will want to initially write tests using the functional-level model. Once these tests are working on the functional-level model, you can move on to testing the baseline and alternative designs.

The following commands illustrate how to run all of tests for the entire project, how to run just the tests for this lab, and how to run just the basic tests we provide on the various designs.

```
% cd ${HOME}/ece4750/lab-groupXX/sim/build
% py.test ..
% py.test ../lab3_mem
```

```
% py.test ../lab3_mem/BlockingCacheFL_test.py
% py.test ../lab3_mem/BlockingCacheBaseRTL_test.py
% py.test ../lab3_mem/BlockingCacheAltRTL_test.py
```

You will add your directed and random tests to `BlockingCacheFL_test.py`. Since this harness is shared across the functional-level model, the baseline design, and the alternative design you can write your tests once and reuse them to test all three models. You will be adding more test cases. Do not just make the given test case larger. A key challenge in writing directed tests for cache memories, is that most of the miss path must be working before you can test the hit path. The miss path is significantly more complicated than the hit path, so this lends itself more towards a monolithic design process. Most of the cache must be implemented before we can run our first directed test. We could potentially use white-box ad-hoc testing that directly initializes the tag and data arrays in the cache before starting the test, but these ad-hoc tests are fragile and difficult to develop on the functional-level model.

To address this challenge, we will use a design-for-test (DFT) approach. DFT involves adding features to a design that are solely meant to facilitate test-driven development. In this specific design, we will be adding a new init transaction to go along with our current read and write transactions. The init transaction does the following:

- Writes to the appropriate cache line based on the index bits of the address
- Writes the corresponding tag
- Never updates main memory
- Sets the valid bit for that cache line to one
- Sets the dirty bit for that cache line to zero
- Sets the `cacheresp`'s test field to zero

Only one init transaction is allowed after reset, and it must be the very first transaction. Using more than one init transaction after reset, or using an init transaction after a read or write transaction is undefined. The staff tests will not test any undefined behavior. If you would like, you can “define” some of the undefined behavior if it facilitates your testing strategy.

Figure 7 illustrates how we will be writing tests for this lab using various helper tasks which are defined in `BlockingCacheFL_test.py`. The `req` and `resp` Python helper functions will create a memory request message and the expected memory response message. We use the test field in response messages to test whether the memory request resulted in a hit or a miss. This specific example first uses an init transaction to initialize one word in the first cache line, before using a read transaction to read this same word. Note that the second transaction should be a hit and we set the second `cacheresp` message's test field to be one. For each test case we define a Python function that returns a list of request-response message pairs. The request messages and response messages will be passed to the test source and the test sink respectively. In Figure 7, lines 6–11 and lines 17–22 illustrate two test cases. We also provide you a helper function to load data into the test memory before running the test. It will allow you to test the cache refill path without involving the cache evict path. If you want to load data into the test memory before running the test, you can create a Python function that returns a list of address-data pairs and then the test function we provide will load it to the test memory before running the test. For example lines 26–31, load the test memory with two words of data at addresses `0x00000000` and `0x00000004` before running the `read_miss_1word_msg` test case.

Once you create a new test harness, you can add it to the test case table, as shown on lines 37–41 in Figure 7. A test case table has eight columns. The first column is the name of tests, the second one is the function that generates source/sink messages, and the third one is the function that generates memory data to be loaded before running the test. If your test case does not need to load data to

```

1  #-----
2  # Test Case: read hit path
3  #-----
4  # The test field in the response message: 0 == MISS, 1 == HIT
5
6  def read_hit_1word_clean( base_addr ):
7      return [
8          # type opq addr len data type opq test len data
9          req( 'in', 0x00, base_addr, 0, 0xdeadbeef ), resp( 'in', 0x00, 0, 0, 0 ),
10         req( 'rd', 0x01, base_addr, 0, 0 ), resp( 'rd', 0x01, 1, 0, 0xdeadbeef ),
11     ]
12
13 #-----
14 # Test Case: read miss path
15 #-----
16
17 def read_miss_1word_msg( base_addr ):
18     return [
19         # type opq addr len data type opq test len data
20         req( 'rd', 0x00, 0x00000000, 0, 0 ), resp( 'rd', 0x00, 0, 0, 0xdeadbeef ),
21         req( 'rd', 0x01, 0x00000004, 0, 0 ), resp( 'rd', 0x01, 1, 0, 0x00c0ffee ),
22     ]
23
24 # Data to be loaded into memory before running the test
25
26 def read_miss_1word_mem( base_addr ):
27     return [
28         # addr data
29         0x00000000, 0xdeadbeef,
30         0x00000004, 0x00c0ffee,
31     ]
32
33 #-----
34 # Test table for generic test
35 #-----
36
37 test_case_table_generic = mk_test_case_table([
38     ( "msg_func", "mem_data_func", "nbank", "stall", "lat", "src", "sink" ),
39     [ "read_hit_1word", read_hit_1word, None, 0, 0.0, 0, 0, 0 ],
40     [ "read_miss_1word_mem", read_miss_1word_msg, read_miss_1word_mem, 0, 0.0, 0, 0, 0 ],
41 ])
42
43 @pytest.mark.parametrize( **test_case_table_generic )
44 def test_generic( test_params, dump_vcd ):
45     msgs = test_params.msg_func( 0 )
46     if test_params.mem_data_func != None:
47         mem = test_params.mem_data_func( 0 )
48     # Instantiate testharness
49     harness = TestHarness( msgs[:2], msgs[1:2],
50                           test_params.stall, test_params.lat,
51                           test_params.src, test_params.sink,
52                           BlockingCacheFL, False )
53     # Load memory before the test
54     if test_params.mem_data_func != None:
55         harness.load( mem[:2], mem[1:2] )
56     # Run the test
57     run_sim( harness, dump_vcd )

```

**Figure 7: Writing Directed Tests** – A portion of the BlockingCacheFL\_test.py file. We create all test cases in this file and use it to test both FL, baseline RTL and alternative RTL model.

the test memory, simply use `None`. The last five columns are for the number of banks (0 or 4), test memory's stall probability, test memory latency, source delay, and sink delay, respectively.

Ideally, we want to use same set of tests to test the FL, baseline RTL, and alternative RTL model. We define all the test cases in `BlockingCacheFL_test.py`, test them on the FL model to make sure the test cases are correct, and we import them in the `BlockingCacheBaseRTL_test.py` and `BlockingCacheAltRTL_test.py` test scripts. We need to be careful about the test field, because the same test may have different hit/miss behavior on different cache implementations. For example, in an FL cache, every response is a miss because we simply pass `cachereq` and `cacheresp` to memory. The alternative design will have less conflict misses than the baseline design, because the alternative design is set-associative whereas the baseline design is direct-mapped. Therefore, we should expect different values for the test field in the `cacheresp` messages passed to the sink from different cache models even if we use the same source messages. To solve this issue, we provide you a custom `TestCacheSink` model which is used by the test harness in `BlockingCacheFL_test.py`. The `TestCacheSink` is similar to the `TestSink` you have used before, except that it can optionally skip checking the test field. Lines 49–52 in Figure 7 show how to instantiate this `TestHarness` model. The first two parameters (`src_msgs` and `sink_msgs`) are source and sink messages. The `stall_prob`, `latency`, `src_delay`, and `sink_delay` parameters are the stalling probability of the test memory, latency (in cycles) of the test memory, source delay, and source delay, respectively. `CacheModel` is the model we want to test. `check_test` determines whether the test harness should check the test field in `cacheresp` messages from the model under test to the test sink. When we run a test case on the FL model, we should set `check_test` to `False` to make the harness skip checking the test field because the test field is always zero for the FL model. Otherwise the test will fail. When we test the actual RTL models, we must set `check_test` to `True` in order to inspect every `cacheresp` message's test field to verify if the request correctly hit or missed in the cache.

As mentioned above, your baseline and alternative designs will have different hit/miss behaviors, so you may need to use different sink values even for the same sequence of source messages. You should add tests designed specifically for your baseline or alternative design. For example, you should have tests that only hit in a two-way set-associative cache to make sure your alternative design is indeed two-way set-associative. We group the test cases into three test case tables. `test_case_table_generic` is shown on lines 37–41 in Figure 7 and is used to generically test both the baseline and alternative designs (i.e., tests in this table should have the same expected behavior for both the baseline and alternative design). `test_case_table_set_assoc` and `test_case_table_set_dir_mapped` are used to test only one of the designs. We provide examples which test for a very simple conflict miss in the baseline design and test for a hit with the same sequence of source messages in the alternative design.

Some suggestions for what you might want to test are listed below. Each of these would probably be a separate test case.

- Read hit path for clean lines
- Write hit path for clean lines
- Read hit path for dirty lines
- Write hit path for dirty lines
- Read miss with refill and no eviction
- Write miss with refill and no eviction
- Read miss with refill and eviction
- Write miss with refill and eviction
- Tests which stress entire cache, not just a few cache lines
- Conflict misses

- Capacity misses
- LRU replacement policy by filling up a way
- Tests for a four-bank cache organization
- Tests specifically designed to trigger corner cases in your alternative design
- Testing all or some of the above using random source and sink delays and test memory delays

Note that you need to test the ability for your cache to be used in a four-bank cache organization. In the test case tables in `BlockingCacheFL_test.py`, there is a column named `nbank`. This parameter is passed to the test harness and then your cache model. You only need to test the cases where `nbank` is zero and four. Think critically about how to discriminate between a correct cache implementation which ignores the bank bits, and an incorrect cache implementation which does not ignore the bank bits. Then design a sequence of memory transactions, some of which hit (or miss) in the wrong implementation but miss (or hit) in the correct implementation.

Once you have finished writing your directed tests you should move on to writing random tests. You can use the same Python-based random test generation system we used in the first lab. Some suggestions for what you might want to test are listed below. Each of these would probably be a separate test pattern, or potentially multiple test patterns with different random parameters.

- Simple address patterns, single request type, with random data
- Simple address patterns, with random request types and data
- Random address patterns, request types, and data
- Unit stride with random data
- Stride with random data
- Unit stride (high spatial locality) mixed with shared (high temporal locality)

Writing random tests for memories can actually be quite challenging. With the first lab, the correct output was trivial to calculate based on the random inputs, but with a memory system the correct output (i.e., the data we expect in a memory read response) depends on the last write to the corresponding address. To write random tests with random address patterns and/or types, you will need to keep track of a “reference memory” in your Python script. This reference memory can just be an array of words. Every time you generate a write request, you should update the reference memory in addition to generating the appropriate write request. Every time you generate a read request, you should consult your reference memory to determine what data we expect to be returned in a memory read response.

You will almost certainly want to use line tracing to visualize the execution of transactions on your baseline and alternative designs. We have provided some line tracing code for you in the test harness which traces the cache request/response and memory request/response interfaces. Figure 8 illustrates a line trace for the basic test in Figure 7 executing on the baseline design with extra annotations to indicate what the columns mean. The first column shows when memory request messages are sent from the test source into the cache, and the last column shows when memory response messages are sent from the cache back to the test sink. The second column shows the state of the cache. This column is critical to understanding the behavior of your cache, but it is not currently implemented in the lab harness. You will need to modify the line tracing code in your baseline and alternative designs to append a string representing the current cache state. Use the short state names as given in the state description list above (e.g., I for `STATE_IDLE`, TC for `STATE_TAG_CHECK`). The third and fourth columns show the memory request and response messages to/from the test memory. Figure 9 illustrates a line trace for a more extensive test that is forcing a line to be evicted. Notice how the line trace clearly shows what data is moving between the test source/sink, cache, and test memory.

cycle	cachreq	state	memreq	memresp	cacheresp
2:		(I )		() .	.
3:	in:00:00001000:deadbeef	(I )		() .	
4:	#	(TC)		() .	
5:	#	(IN)		() .	
6:	#	(W )		() .	in:00:0:
7:	rd:01:00001000:	(I )		() .	
8:	.	(TC)		() .	
9:	.	(RD)		() .	
10:	.	(W )		() .	rd:01:1:deadbeef

**Figure 8: Line Trace for Basic Directed Test** – The line trace shows two memory requests sent from the test source to the cache, the four states each transaction goes through, and then the response being sent from the cache back to the test sink.

cycle	cachreq	state	memreq	memresp	cacheresp
2:		(I )		() .	.
3:	rd:00:00000010:	(I )		() .	
4:	#	(TC)		() .	
5:	#	(RR)	rd:00:00000010:	() .	
6:	#	(RW)		()rd:00:0:00...00	
7:	#	(RU)		() .	
8:	#	(RD)		() .	
9:	#	(W )		() .	rd:00:0:00000000
10:	wr:01:00000010:deadbeef	(I )		() .	
11:	#	(TC)		() .	
12:	#	(WD)		() .	
13:	#	(W )		() .	wr:01:1:
14:	rd:02:00000110:	(I )		() .	
15:	.	(TC)		() .	
16:	.	(EP)		() .	
17:	.	(ER)	wr:00:00000010:00...deadbeef	() .	
18:	.	(EW)		()wr:00:0:	
19:	.	(RR)	rd:00:00000110:	() .	
20:	.	(RW)		()rd:00:0:00...00	
21:	.	(RU)		() .	
22:	.	(RD)		() .	
23:	.	(W )		() .	rd:02:0:cafecafe

**Figure 9: Line Trace for More Involved Directed Test** – The line trace shows three memory requests meant to trigger an eviction of a dirty line. Notice how the third request must go through a total of 10 states as the FSM does tag check, eviction, and refill. Note, only a portion of the bits for the data field for memory request/responses are shown for simplicity.

In addition to the tests for the entire cache, you must also add additional unit tests for any datapath components you add or modify.

## 5. Evaluation

Once you have verified the functionality of the baseline and alternative designs, you should then use the provided simulator to evaluate these two designs. The simulator delays all responses from the test memory by 20 cycles to model a long main-memory latency. You can run the simulator to see the performance of each cache implementation as follows:

```
% cd ${HOME}/ece4750/lab-groupXX/sim/build
% ../lab3_mem/mem-sim --impl base --pattern loop-1d --stats
% ../lab3_mem/mem-sim --impl alt --pattern loop-1d --stats
```

We provide you with three input patterns that capture common access patterns in loops. The C code for each loop that might generate the corresponding pattern is shown in Figure 10. The `loop-1d` pattern simply iterates through an array. The `loop-2d` pattern iterates through the same array five times. The `loop-3d` pattern uses a more interesting stride to iterate through an array multiple times.

The simulator will display a collection of statistics: number of cycles, number of memory and cache accesses, number of misses, miss rate, and the average memory access latency (AMAL). You should study the line traces (with the `--trace` option) and possibly the waveforms (with the `--dump-vcd` option) to understand the reason why each design performs as it does on the various patterns.

You can run simulations for all given patterns like this:

```
% cd ${HOME}/ece4750/lab-groupXX/sim/build
% python ../lab3_mem/mem_sim_eval.py
```

You must add additional evaluation patterns with different amounts of spatial and temporal locality. We strongly recommend including some patterns that mix reads/writes and random patterns. We recommend a total of six or more patterns for evaluation. Obviously, these patterns need to be carefully chosen to highlight the differences between the baseline and alternative designs. You will also need to add the name of the new dataset to the `mem-sim` simulator script.

Writing an access pattern for the simulator is similar to writing a test case. Basically for each pattern you need to write a Python function that returns a list of source messages, a list of sink message, and a list of memory address-data pairs that will be loaded to the test memory before the simulation. Figure 11 shows you `loop-3d` pattern. Please keep in mind that patterns you will write in the simulator are not for testing. Instead, you need to fully test your designs using test cases and then use patterns in the simulator script as a way to evaluate your designs.

## 6. Looking Towards the Multicore System in Lab 5

In lab 5, we will compose the pipelined processor and cache memory designed in labs 2–3 to create a baseline single-core system, and we will compose the pipelined processor, cache memory, and bus network designed in labs 2–4 to create the alternative multicore system. You will be developing a serial and parallel sorting microbenchmark, and comparing the performance of this microbenchmark across the baseline and alternative designs. You will quickly find that the performance of your alternative multicore system is limited by the hit latency of the cache you designed in this lab. While we could move to a more aggressive pipelined cache microarchitecture, you can achieve much of the same benefit by simply merging states in the FSM control unit used in this lab. Ideally, you would merge enough states to enable a single-cycle hit latency for reads (i.e., a single state for read hits) and a sustained throughput of one read hit per cycle. This requires performing tag check and data access in parallel, and carefully handling the `val/rdy` signals for the cache request and response interfaces. Writes can potentially use two states to do tag check and data access in sequence, although single-

```

// loop-1d pattern      // loop-2d pattern      // loop-3d pattern
for ( i = 0; i < 100; i++ )  for ( i = 0; i < 5; i++ )  for ( i = 0; i < 5; i++ )
    result += a[i];          for ( j = 0; j < 100; j++ )  for ( j = 0; j < 2; j++ )
                              result += a[j];          for ( k = 0; k < 8; k++ )
                              result += a[j*64 + k*4];

```

**Figure 10: Evaluation Patterns** – Three loops that correspond to the given evaluation patterns.

```

1  #-----
2  # Pattern: loop-3d
3  #-----
4
5  def loop_3d():
6      src_msgs = []
7      sink_msgs = []
8
9      mem_data = []
10     mem_word = Bits( 32 )
11
12     # Initialize memory
13     addr = 0
14     for i in xrange( 2 ):
15         for j in xrange( 8 ):
16             addr = i*256 + j*16
17             mem_word.value = i*64 + j*4
18             mem_data.append( addr )
19             mem_data.append( mem_word.uint() )
20             addr += 4
21
22     # Read from memory
23     for i in xrange( 5 ):
24         for j in xrange( 2 ):
25             for k in xrange( 8 ):
26                 addr = j*256 + k*16
27                 data = j*64 + k*4
28                 src_msgs.append( mk_req ( 0, addr, 0, 0 ) )
29                 sink_msgs.append( mk_resp( 0, 0, data ) )
30
31     return [ src_msgs, sink_msgs, mem_data ]

```

**Figure 11: loop-3d Pattern for the Simulator** – A function that returns source messages, sink messages, and a memory section for loop-3d access pattern.

cycle hit latency for writes is still possible if the cache response is sent back in the first state. Reducing the read hit latency is the most critical since this would improve the performance of instruction fetch in your processor. There is no need to wait until lab 5. Students should feel free to start optimizing their cache as part of the alternative design in this lab, or after this lab is submitted.

## Acknowledgments

This lab was created by Shunning Jiang, Shuang Chen, Ian Thompson, Moyang Wang, Christopher Torng, Berkin Ilbeyi, Ackerley Tng, Shreesha Srinath, Christopher Batten, and Ji Kim as part of the course ECE 4750 Computer Architecture at Cornell University.